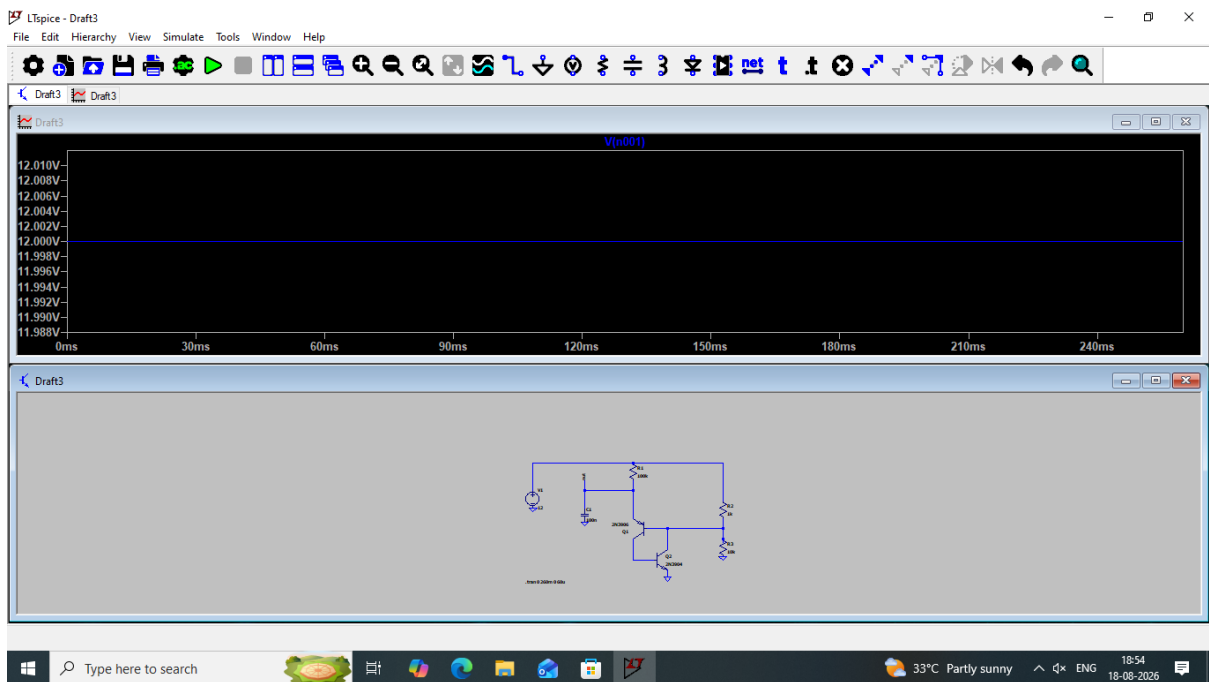


EXPERIMENT – 5

DESIGN AND SIMULATION OF UJT RELAXATION OSCILLATOR USING LTSPICE

INPUT WAVEFORM:



OUTPUT WAVEFORM:

