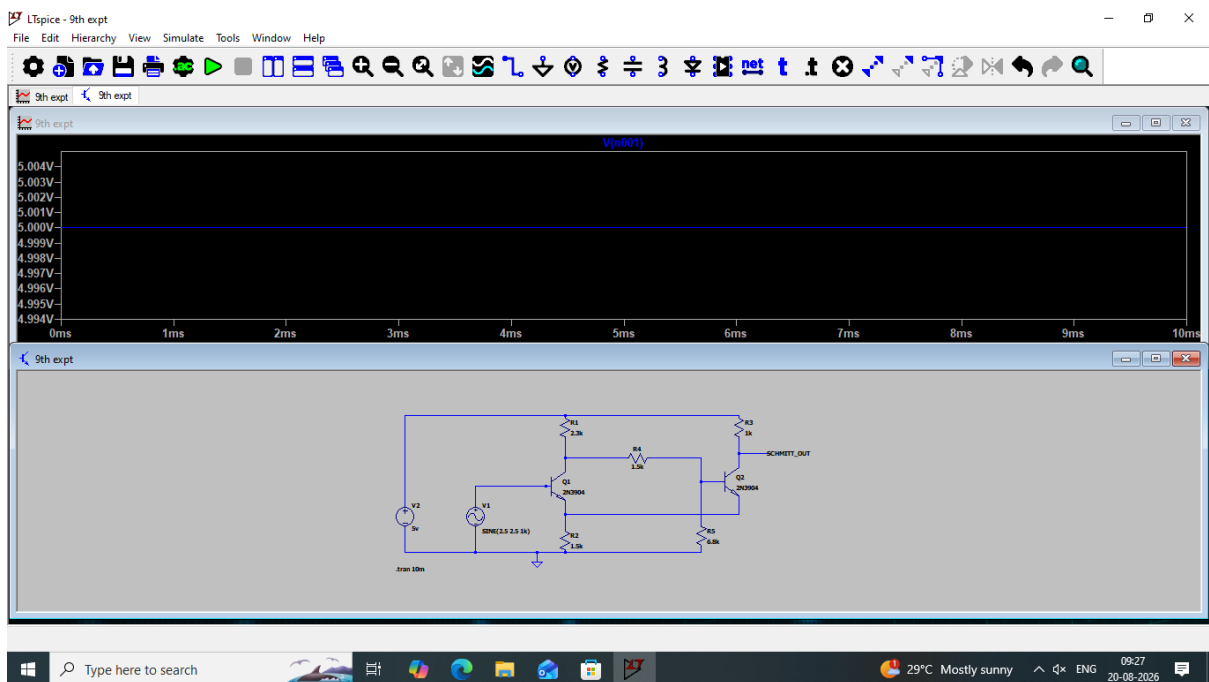


A.V.KAVERI,
192512188.

EXPERIMENT – 9

Design and Simulation of Schmitt Trigger using LT Spice Simulator

INPUT WAVEFORM



OUTPUT WAVEFORM

