

**NAME: A.V.KAVERI**

**REG.NO: 192512188**



**COURSE CODE: ECA0404**


**COURSE NAME: ANALOG CIRCUITS**

**PRACTICAL LAB RESULTS**

## EXPERIMENT – 10 Design of Hartley Oscillator Using PCB Software

### Circuit Diagram

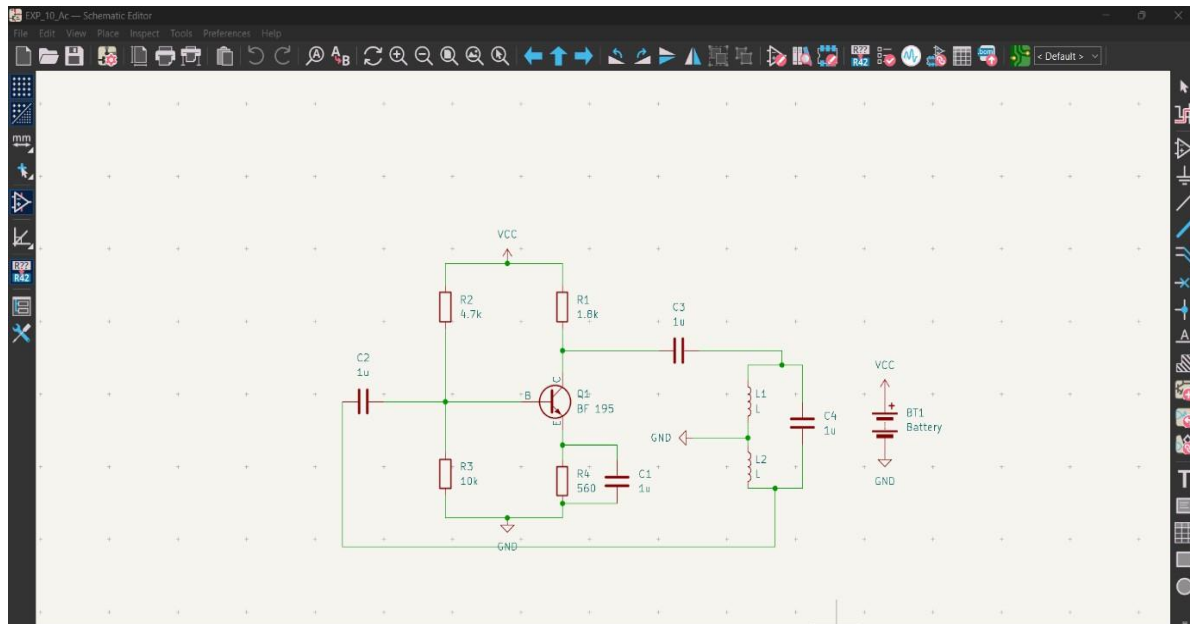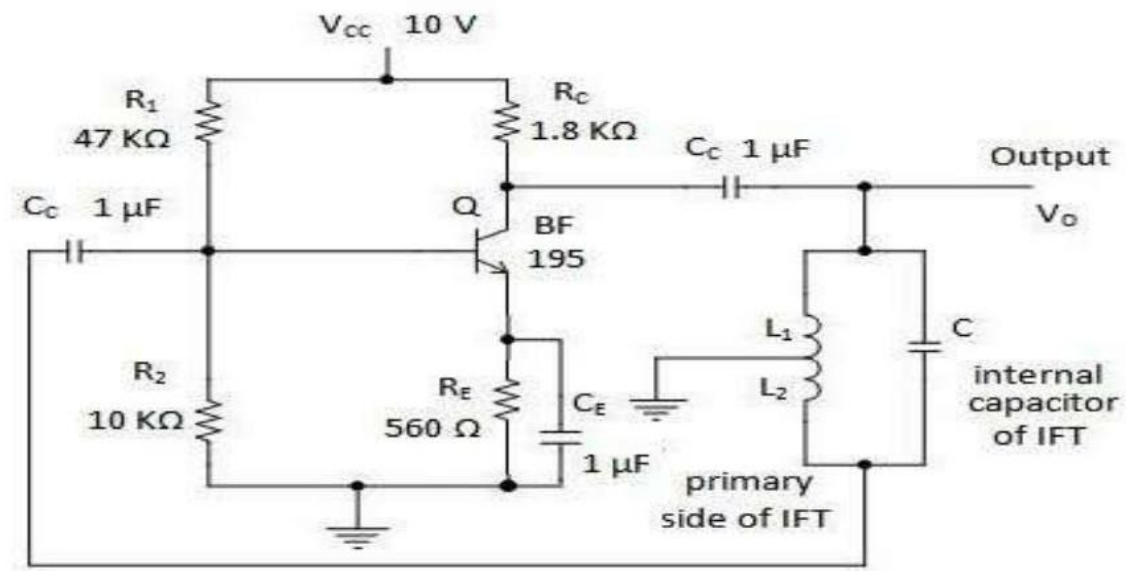

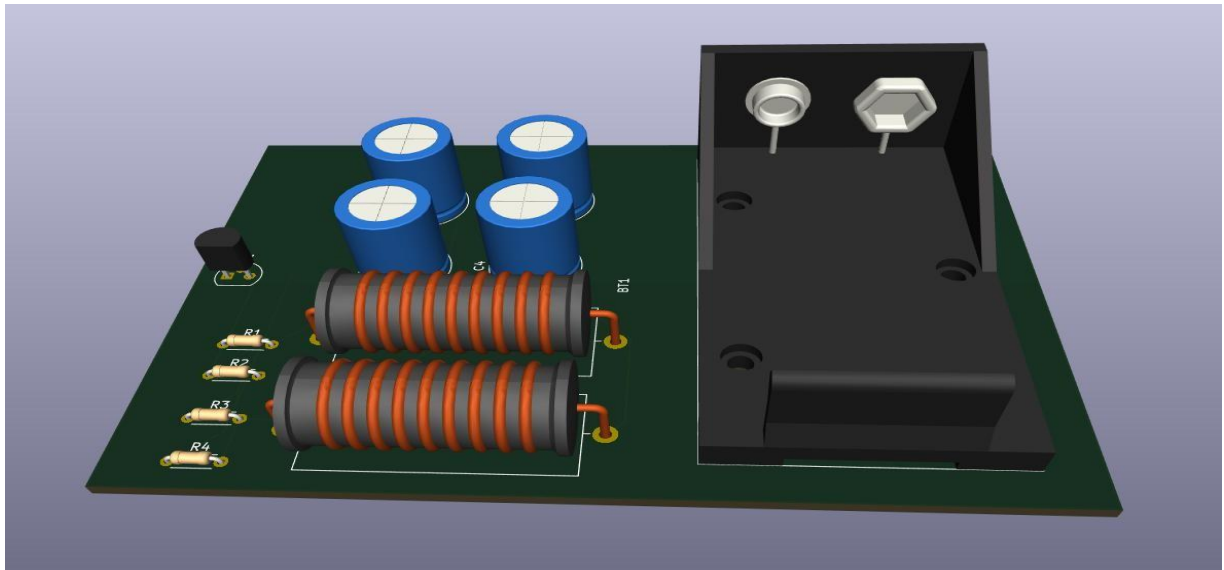

| Name                                                                                                           | Date modified    | Type        | Size  |
|----------------------------------------------------------------------------------------------------------------|------------------|-------------|-------|
|  EXP_10_Ac-B_Cu.gbr           | 21-08-2026 08:21 | GBR File    | 4 KB  |
|  EXP_10_Ac-B_Mask.gbr         | 21-08-2026 08:21 | GBR File    | 2 KB  |
|  EXP_10_Ac-B_Paste.gbr       | 21-08-2026 08:21 | GBR File    | 1 KB  |
|  EXP_10_Ac-B_Silkscreen.gbr | 21-08-2026 08:21 | GBR File    | 1 KB  |
|  EXP_10_Ac-Edge_Cuts.gbr    | 21-08-2026 08:21 | GBR File    | 1 KB  |
|  EXP_10_Ac-F_Cu.gbr         | 21-08-2026 08:21 | GBR File    | 5 KB  |
|  EXP_10_Ac-F_Mask.gbr       | 21-08-2026 08:21 | GBR File    | 2 KB  |
|  EXP_10_Ac-F_Paste.gbr      | 21-08-2026 08:21 | GBR File    | 1 KB  |
|  EXP_10_Ac-F_Silkscreen.gbr | 21-08-2026 08:21 | GBR File    | 14 KB |
|  EXP_10_Ac-job.gbrjob       | 21-08-2026 08:21 | GBRJOB File | 3 KB  |

